

# Circuit Theory and Electronics Fundamentals

## T2

Physics Engineering, Técnico, University of Lisbon

April 5, 2021

### Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Theoretical Analysis</b>	<b>2</b>
2.1	For $t < 0$ . . . . .	3
2.2	For $t = 0$ . . . . .	3
2.3	Natural Solution . . . . .	5
2.4	Forced Solution . . . . .	5
2.5	Natural and Forced Superimposed . . . . .	6
2.6	Frequency Response . . . . .	7
<b>3</b>	<b>Simulation Analysis</b>	<b>9</b>
3.1	For $t < 0$ . . . . .	9
3.2	For $t = 0$ . . . . .	9
3.3	Natural Solution . . . . .	11
3.4	Total Solution . . . . .	11
3.5	Frequency Response . . . . .	12
<b>4</b>	<b>Conclusion</b>	<b>13</b>

### 1 Introduction

The goal of this laboratory assignment is to study and analyse a RC circuit composed by a dependent current source, a capacitor, resistors, and lastly, one dependent and one independent voltage source to find the natural and forced response and frequency analysis of the said circuit. A comparison will be done between the NgSpice simulation and the theoretical analysis of the circuit.

The main objective will be to further learn about both methods of analysis, learning about their similarities, differences and which positive and negative sides each of them have.

The circuit is represented with resort to *LibreOffice Draw* and can be viewed in figure 1.

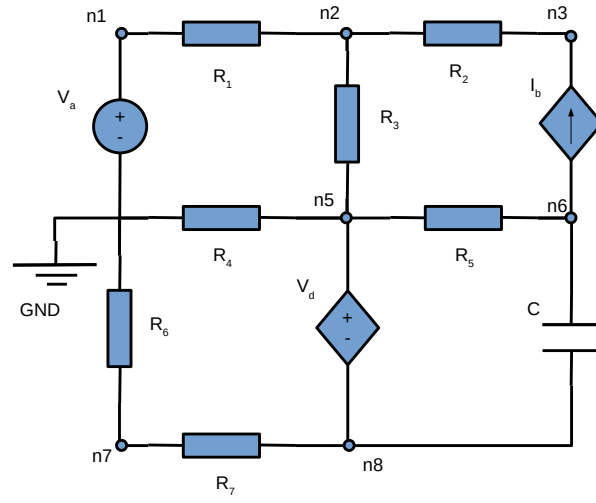


Figure 1: Studied Circuit

In Section 2, a theoretical analysis of the circuit is presented. In Section 3, the circuit is analysed by simulation, and the results are compared to the theoretical results obtained in Section 2. The conclusions of this study are outlined in Section 4.

## 2 Theoretical Analysis

In this section, the circuit shown in Figure 1 is analysed theoretically. The known values in  $k\Omega$ ,  $V$ ,  $mS$ ,  $\mu F$  can be checked in the table below.

$R_1$	1.02362892933
$R_2$	2.08640382129
$R_3$	3.09996108706
$R_4$	4.08183334334
$R_5$	3.04169575790
$R_6$	2.04156679366
$R_7$	1.04156790057
$C$	1.04908336809
$K_b$	7.29571922963
$K_d$	8.16840649221

Table 1: Known Data

## 2.1 For $t < 0$

For  $t < 0$ ,  $v_s = V_s$ , according to the given equation. Furthermore the capacitor acts like an open circuit since it is fully charged and no current goes through it. Therefore,  $I_c = 0$ .

Applying the node method, it is possible to solve the circuit with the information upwards, since all the other information is given in 1. The system used to solve this circuit is shown below.

$$\begin{cases} V_1 = V_s \\ V_d = V_5 - V_8 \\ V_b = V_2 - V_5 \\ \frac{V_7 K_d}{R_6} = V_d \\ \frac{V_1 - V_2}{R_1} + \frac{V_3 - V_2}{R_2} - \frac{V_5 - V_2}{R_3} = 0 \\ \frac{V_2 - V_3}{R_2} - K_b V_b = 0 \\ \frac{-V_7}{R_6} + \frac{V_8 - V_7}{R_7} = 0 \\ \frac{V_7 - V_8}{R_7} - \frac{V_5}{R_4} + \frac{V_6 - V_5}{R_5} + \frac{V_2 - V_5}{R_3} = 0 \\ \frac{V_5 - V_6}{R_5} + K_b V_b = 0 \end{cases}$$

Using Octave software it was possible to collect the data shown in table 2 and 3.

$V_1$	5.178860
$V_2$	4.933049e+00
$V_3$	4.408850e+00
$V_5$	4.967487e+00
$V_6$	5.731699e+00
$V_7$	-1.994280e+00
$V_8$	-3.011723e+00
$V_b$	3.443737e-02
$V_d$	-7.979210e+00
$V_s$	5.178860e+00

Table 2: Voltages in all nodes in V

$I_1$	-0.240136
$I_2$	2.512454e-01
$I_3$	1.110897e-02
$I_4$	1.216974e+00
$I_5$	2.512454e-01
$I_6$	-9.768380e-01
$I_7$	-9.768380e-01
$I_b$	2.512454e-01
$I_d$	-9.768380e-01
$I_s$	-2.401364e-01

Table 3: Currents in all branches in mA

The voltages and currents were then calculated.

## 2.2 For $t = 0$

In order to solve the second exercise, firstly it is necessary to replace the capacitor by a voltage source  $V_x$ , which will impose a voltage of exactly what was determined for the capacitor

in the first exercise. This is the first step to compute de  $R_{eq}$  as seen from the capacitor because now it is possible to run a new nodal analysis with  $v_s$  set to 0 in order to determine  $I_x$ , which is the current that goes through the capacitor.

Solving the matrix below it is possible to determine the values in 2.2 and thus determine  $R_{eq}$ .

Compute  $R_{eq}$  is fundamental because this allows to determine the natural solution of the system through the  $RC$  constant. This application will be demenstrated in the next exercise.

$$\begin{cases} V_1 = V_s \\ V_d = V_5 - V_8 \\ V_b = V_2 - V_5 \\ V_x = V_6 - V_8 \\ \frac{V_7 K_d}{R_6} = V_d \\ \frac{V_1 - V_2}{R_1} + \frac{V_3 - V_2}{R_2} - \frac{V_5 - V_2}{R_3} = 0 \\ \frac{V_2 - V_3}{R_2} - K_b V_b = 0 \\ \frac{-V_7}{R_6} - \frac{V_8 - V_7}{R_7} = 0 \\ \frac{V_7 - V_8}{R_7} - \frac{V_5}{R_4} + \frac{V_6 - V_5}{R_5} + \frac{V_2 - V_5}{R_3} - \frac{V_x}{R_{eq}} = 0 \\ \frac{V_5 - V_6}{R_5} + K_b V_b + \frac{V_x}{R_{eq}} = 0 \end{cases}$$

Through Octave it was possible to collect the data shown in table 4 and 5.

$V_1$	0.000000
$V_2$	-6.049490e-16
$V_3$	-1.440730e-15
$V_5$	-1.195182e-15
$V_6$	8.743422e+00
$V_7$	1.804316e-15
$V_8$	2.724843e-15
$V_b$	5.490679e-17
$V_d$	3.920025e-15
$V_s$	0.000000e+00
$V_x$	8.743422e+00

Table 4: Voltages in all nodes in V

$I_1$	-0.000000
$I_2$	7.525891e-18
$I_3$	-1.904001e-16
$I_4$	-2.928052e-16
$I_5$	2.874522e+00
$I_6$	4.799008e-16
$I_7$	4.799008e-16
$I_b$	4.005845e-16
$I_d$	4.799008e-16
$I_s$	-5.909846e-16
$I_x$	2.874522e+00

Table 5: Currents in all branches in mA

The value for  $V_x$  was established as  $V_6 - V_8$  being  $V_6$  and  $V_8$  determined in the previous section.

## 2.3 Natural Solution

Now the task was to determine the natural solution for  $V_6$ . Using  $V_x$ , determined in the previous exercise, as the initial condition, it was possible, applying 1, since this is a RC circuit, to determine the natural solution, plotted in figure 2.

$$V_{6n} = Ae^{\frac{-t}{\tau}} \quad \tau = R_{eq}C \quad (1)$$

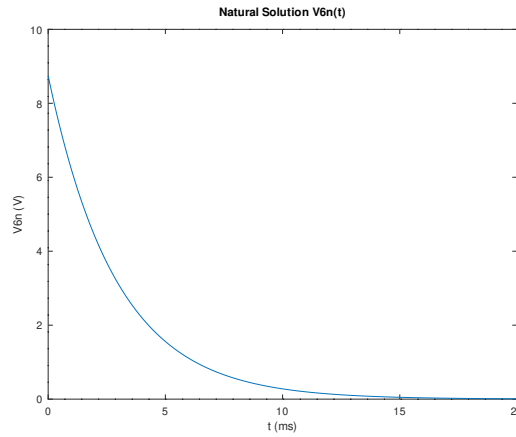


Figure 2: Natural Solution

## 2.4 Forced Solution

For this section of the analysis, one was asked to find the forced solution  $V_6 f(t)$  for a frequency of 1000Hz. In order to simplify the calculations, and as suggested, a phasor with constant  $V_s$  of 1V was used. A similar node analysis was ran, using  $V_s$  as the voltage source, and replacing the capacitance of capacitor  $C$  with its impedance  $Z$ . Like so, the following nodal equations were derived:

$$Z_c = \frac{1}{j\omega C} \quad \omega = 2\pi f \quad (2)$$

$$\begin{cases} V_1 = V_s \\ V_d = V_5 - V_8 \\ V_b = V_2 - V_5 \\ \frac{V_7 K_d}{R_6} = V_d \\ \frac{V_1 - V_2}{R_1} + \frac{V_3 - V_2}{R_2} - \frac{V_5 - V_2}{R_3} = 0 \\ \frac{V_2 - V_3}{R_2} - K_b V_b = 0 \\ \frac{-V_7}{R_6} - \frac{V_8 - V_7}{R_7} = 0 \\ \frac{V_7 - V_8}{R_7} - \frac{V_5}{R_4} + \frac{V_6 - V_5}{R_5} + \frac{V_2 - V_5}{R_3} - \frac{V_6 - V_8}{Z_c} = 0 \\ \frac{V_5 - V_6}{R_5} + K_b V_b + \frac{V_8 - V_6}{Z_c} = 0 \end{cases}$$

Splitting the complex numbers and determining the angles and the modules, the two following tables were made with the following equations:

$$V_{complex_i} = V_i e^{-j\text{phase}(i)} \quad (3)$$

With angle and abs commands in octave we were able to calculate the following values.

$V_1$	1.000000e+00
$V_2$	9.531327e-01
$V_3$	8.616507e-01
$V_5$	9.471228e-01
$V_6$	5.742283e-01
$V_7$	3.802382e-01
$V_8$	5.742283e-01

Table 6: Complex Amplitudes

$Ph_1$	0.000000e+00
$Ph_2$	-3.749681e-21
$Ph_3$	-1.224400e-20
$Ph_5$	-4.257358e-21
$Ph_6$	3.141434e+00
$Ph_7$	3.141593e+00
$Ph_8$	3.141593e+00

Table 7: Phases

Therefore, we can state that:

$$V_6 = 5.742283e - 01e^{-j3.141434e+00} \quad (4)$$

## 2.5 Natural and Forced Superimposed

By converting the phasor to real time functions, a function to evaluate  $V_6$ , for  $t > 0$ , was found by simply adding the natural and forced solutions, previously calculated for a frequency of 1000Hz. On the other hand, the equation for  $V_s(t)$  for  $t > 0$  was already implicit on the initial circuit diagram. Both equations are written below.

$$V_{ifinal} = V_{in} + V_{if} \quad (5)$$

So, calculating  $V_{6final}$ :

$$V_6(t) = e^{\frac{-t}{R_{eq}C}} + A e^{-j\text{phase}(i)} \quad (6)$$

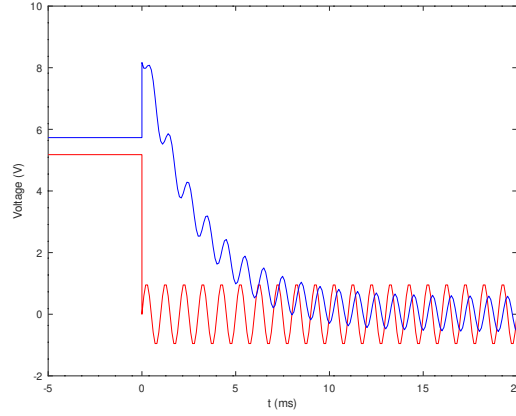


Figure 3: Natural and Forced Superimposed

## 2.6 Frequency Response

The graphs for phase and magnitude were plotted. The magnitude in dB is calculated with the help of the function `abs` and in a logarithmic scale, multiplied by the 20. The phase in degrees is calculated with the function `angle` and there has to be a conversion from rad to degrees.

$$Z = \frac{1}{j2\pi fC} \quad (7)$$

with  $f$  being a logarithmic scale vector from -6 to 6 with 200 entries.

The system used was:

$$\begin{cases} V_1 = V_s \\ V_d = V_5 - V_8 \\ V_b = V_2 - V_5 \\ \frac{V_7 K_d}{R_6} = V_d \\ \frac{V_1 - V_2}{R_1} + \frac{V_3 - V_2}{R_2} - \frac{V_5 - V_2}{R_3} = 0 \\ \frac{V_2 - V_3}{R_2} - K_b V_b = 0 \\ \frac{-V_7}{R_6} - \frac{V_8 - V_7}{R_7} = 0 \\ \frac{V_7 - V_8}{R_7} - \frac{V_5}{R_4} + \frac{V_6 - V_5}{R_5} + \frac{V_2 - V_5}{R_3} - \frac{V_6 - V_8}{Z} = 0 \\ \frac{V_5 - V_6}{R_5} + K_b V_b + \frac{V_8 - V_6}{Z} = 0 \end{cases}$$

The complex variables  $V_s fre(k)$ ,  $V_x fre(k)$  and  $V_6 fre(k)$  were assigned and equalled to the just calculated  $V_1$ ,  $V_6 - V_8$  and  $V_6$ , respectively.

The two following graphics were plotted using a base 10 logarithmic scale for frequencies, the logarithmic value of the `abs` of the variables stated above and the angle of these complex variables, converted to degrees.

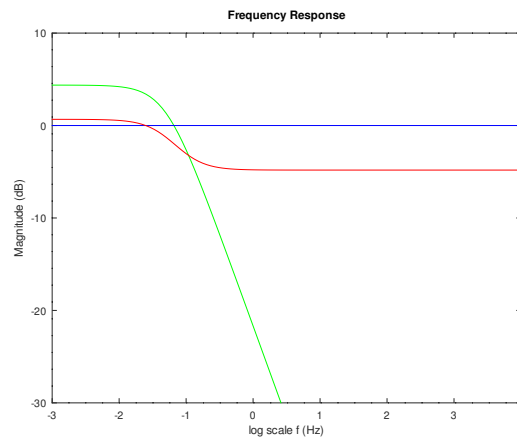


Figure 4: Magnitude (dB) / Frequency (Hz)

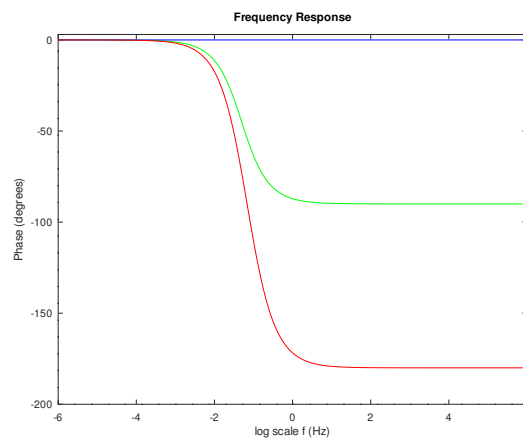


Figure 5: Phase (degrees) / Frequency (Hz)



### 3 Simulation Analysis

#### 3.1 For $t < 0$

The first simulation using ngspice, was an equivalent simulation to the circuit solved theoretical in the first exercise. Notice that an extra voltage source was introduced with only the purpose to serve as an ammeter, controlling the current for the dependent voltage source. The results are shown in the table 8 that will serve to compare with the results obtained.

Name	Value [A or V]
@c1[i]	0.000000e+00
@g1[i]	-2.51245e-04
@r1[i]	-2.40136e-04
@r2[i]	-2.51245e-04
@r3[i]	-1.11090e-05
@r4[i]	1.216975e-03
@r5[i]	2.512453e-04
@r6[i]	-9.76838e-04
@r7[i]	-9.76838e-04
n1	5.178860e+00
n2	4.933049e+00
n3	4.408850e+00
n5	4.967487e+00
n6	5.731699e+00
n7	-1.99428e+00
n8	-3.01172e+00
n9	0.000000e+00

Table 8: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

#### 3.2 For $t = 0$

The second simulation is conducted with the goal to determine  $I_x$ . This is made by setting  $v_s$  to 0 and turning the capacitor into a voltage source  $V_x$  which imposes the same potential between n6 and n8 as the capacitor and operating at  $t = 0$ .

The results below are the results obtained in the simulation. This simulation is not only needed as essential because with  $V_x$  and  $I_x$  we will be able to determine the natural response of the system in the next steps.

Name	Value [A or V]
@g1[i]	0.000000e+00
@r1[i]	0.000000e+00
@r2[i]	0.000000e+00
@r3[i]	0.000000e+00
@r4[i]	0.000000e+00
@r5[i]	2.874522e-03
@r6[i]	0.000000e+00
@r7[i]	0.000000e+00
n1	0.000000e+00
n2	0.000000e+00
n3	0.000000e+00
n5	0.000000e+00
n6	8.743422e+00
n7	0.000000e+00
n8	0.000000e+00
n9	0.000000e+00

Table 9: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

### 3.3 Natural Solution

In the third simulation we use the simulator to perform a transient analysis. For this some initial conditions were given to the software which then realized the analysis. The graphics shown represent the transient analysis for the node n6 between [0,20]ms.

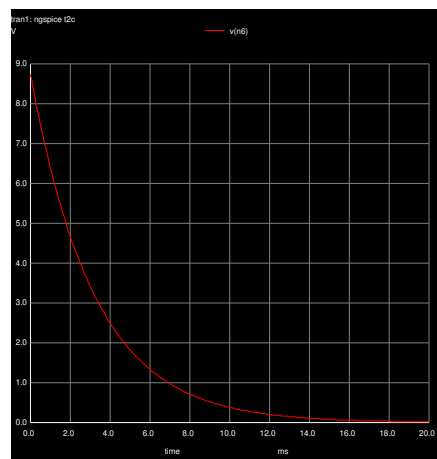


Figure 6: Natural Solution

### 3.4 Total Solution

The simulation conducted next tried to simulate the total response of the node n6. Imposing the conditions given in the exercise, a report showing the response and the stimulus (which was a analysis in n1) is represented in 7.

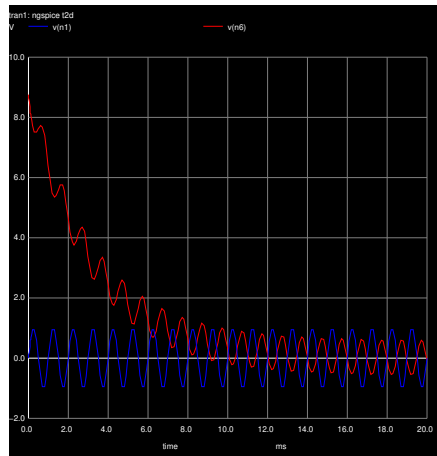


Figure 7: Total Solution

### 3.5 Frequency Response

At last, a frequency analysis was made in order to compare the frequency response between  $v_s$  and  $n6$ . The following graphics were obtained.

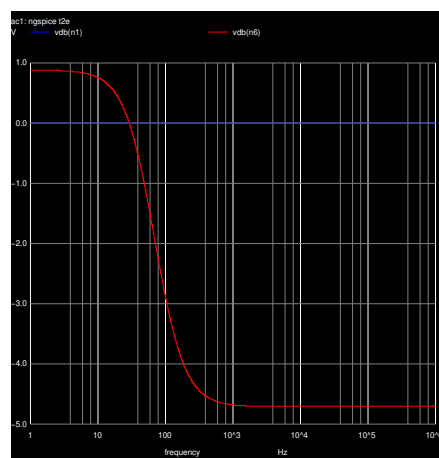


Figure 8: Magnitude

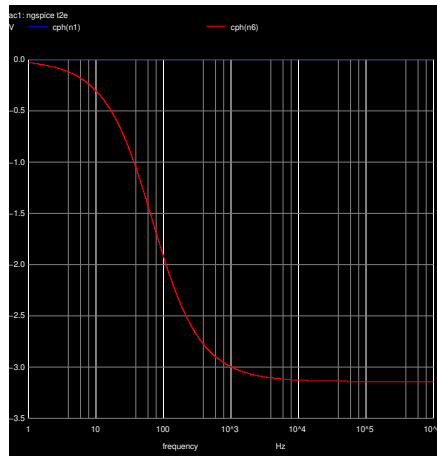


Figure 9: Phase

We noticed a significant difference between them. The frequency response in  $V_s$  is null in opposite to the one seen in  $n6$ . This is due to the fact that  $V_s$  changes according to the frequency, thus remaining constant.  $V_6$  on the other hand changes its value according to  $V_s$  showing a frequency analysis that changes through time.

## 4 Conclusion

As for the first lab experiment, the values for current in branches, voltage in nodes and the equivalent resistance calculated through the simulation made with Ngspice and the theoretical analysis with nodal method in Octave tools were in perfect harmony. The differences between the obtained values are negligible. This is due to the fact that the circuit is also linear, because the capacitor is a linear element.

We can agree that the assignment was completed with success.